



Pic. 3.18 a-Electronic diagram of the detector (TRF) radio receiver with audio amplifier built around the LM386 IC

