
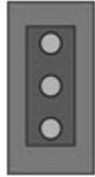







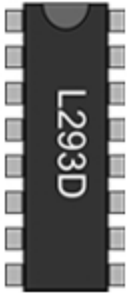


























Circuits and Components Checklist

| Component | Picture | Symbol | Breadboard holes | Note | Added to breadboard? |
|-----------------------|---|---|---|--|--------------------------|
| Power switch |  |  | F1, F2, F3 | Direction it is facing does not matter, but make sure to slide switch down (towards row 30, away from row 1), this is the "off" position | <input type="checkbox"/> |
| Jumper wire |  |  | J2 to (+) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | Left side (+) bus to right side (+) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | Left side (-) bus to right side (-) bus | Color does not matter | <input type="checkbox"/> |
| H-bridge motor driver |  |  | Left side: holes E15 to E22 Right side: holes F15 to F22 | The semi-circular "notch" in one end of the chip must face up (towards row 15). You may need to bend the pins together slightly to get them to fit into the breadboard | <input type="checkbox"/> |
| 10 kΩ resistor |  |  | J16 to (-) bus | Brown, black, orange, gold stripes. Direction does not matter. | <input type="checkbox"/> |
| 10 kΩ resistor |  |  | J21 to (-) bus | Brown, black, orange, gold stripes. Direction does not matter. | <input type="checkbox"/> |

| Component | Picture | Symbol | Breadboard holes | Note | Added to breadboard? |
|------------------------|---|---|------------------|--|--------------------------|
| 10 k Ω resistor |  |  | A16 to (-) bus | Brown, black, orange, gold stripes. Direction does not matter. | <input type="checkbox"/> |
| 10 k Ω resistor |  |  | A21 to (-) bus | Brown, black, orange, gold stripes. Direction does not matter. | <input type="checkbox"/> |
| Jumper wire |  |  | J15 to (+) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | J18 to (-) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | J19 to (-) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | J22 to (+) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | A15 to (+) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | A18 to (-) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | A19 to (-) bus | Color does not matter | <input type="checkbox"/> |
| Jumper wire |  |  | A22 to (+) bus | Color does not matter | <input type="checkbox"/> |


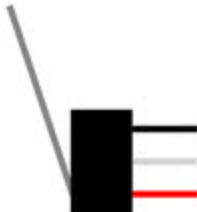

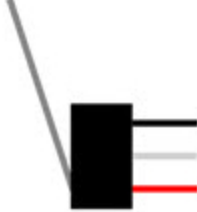








| Component | Picture | Symbol | Breadboard holes | Note | Added to breadboard? |
|---------------------|---|---|---|---|--------------------------|
| Top lever switch |  |  | Red wire to (+) bus Black wire to B21 White wire to B16 | See Figures 6 and 7 for mounting instructions | <input type="checkbox"/> |
| Bottom lever switch |  |  | Red wire to (+) bus Black wire to I21 White wire to I16 | See Figures 6 and 7 for mounting instructions | <input type="checkbox"/> |
| Top motor |  |  | Red lead to H17 Black lead to H20 | When the robot is driving forward, this is the "right" motor. | <input type="checkbox"/> |
| Bottom motor |  |  | Red lead to C17 bus Black lead to C20 | When the robot is driving forward, this is the "left" motor. | <input type="checkbox"/> |
| Battery holder |  |  | Red lead to J1 Black lead to (-) bus | Do not insert batteries until circuit is complete | <input type="checkbox"/> |
| AA battery |  |  | N/A | Insert into battery holder. Make sure (+) signs on batteries line up with (+) signs in battery holder | <input type="checkbox"/> |

Table 2. List of circuit components and locations.

Copyright © 2002-2015 Science Buddies. All rights reserved.

You may print and distribute up to 200 copies of this document annually, at no charge, for personal and classroom educational use.

When printing this document, you may NOT modify it in any way. For any other use, please contact Science Buddies.