



Figure 2. This diagram shows how the circuit should be built. Use alligator clips to connect the multimeter, battery, and conductance sensor. Make sure to connect the *negative* terminal of the battery with the positive terminal of the multimeter in order for the circuit to work.